

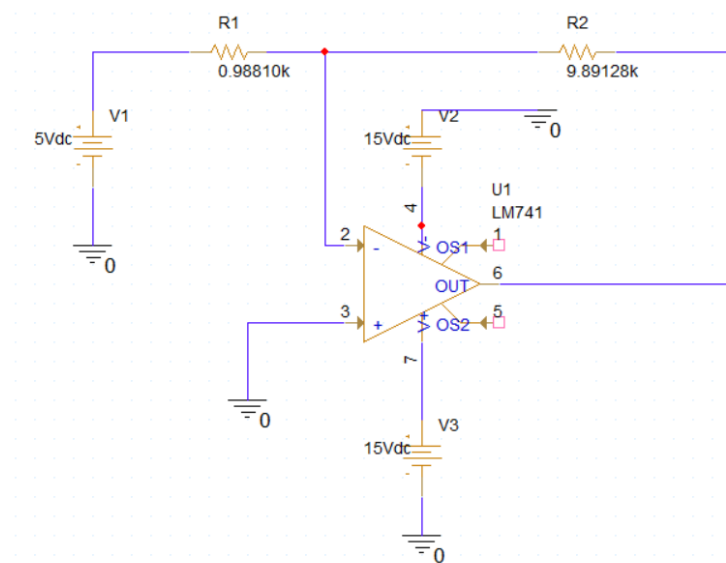


ECE 121 Lab #4

Experiment 1

Experiment 1		Calculated	Measured	Simulated			
Vs=1V	Vo	Vo=-10.01V	Vo=0.010mV	Vo=14.815V		Value	Actual Value
	Vx	Vx=0V	Vx=0.003mV	Vx=-7.7462	Resistor 1	1k	0.98810k
	I1	I1=1.012mA	I1=1.0246mA	I1=-2.2809mA	Resistor 2	10k	9.89128K
	I2	I2=1.012mA	I2=1.0237mA	I2=-2.2809mA			
Vs=5V	Vo	Vo=-50.0519V	Vo=0.019mV	Vo=14.815V			
	Vx	Vx=0V	Vx=0.007mV	Vx=-7.7462			
	I1	I1=5.0602mA	I1=1.6472mA	I1=-2.2809mA			
	I2	I2=5.0602mA	I2=1.6471mA	I2=-2.2809mA			

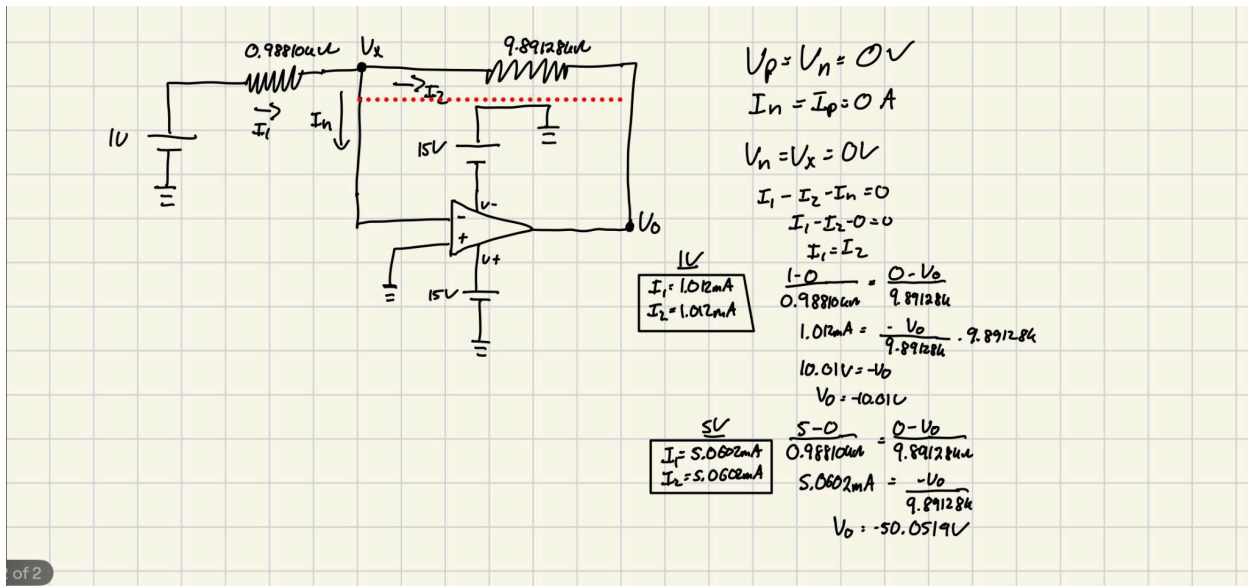



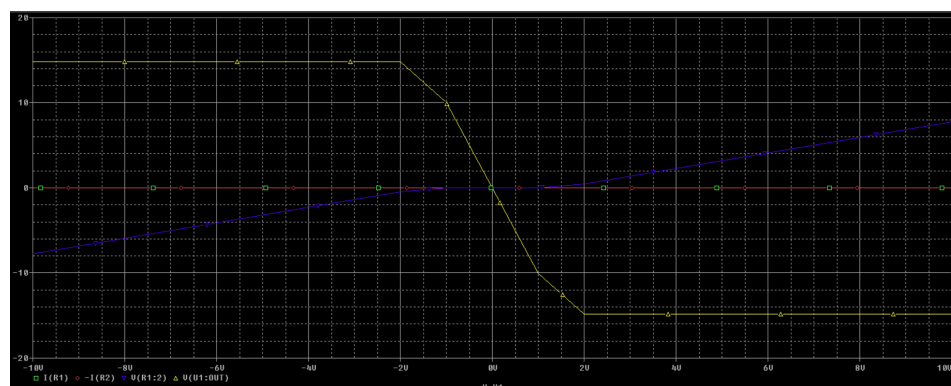


	Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)		0.000		
		X Values	-10.000	-10.000	0.000	Y1 - Y1(Cursor1)	Y2 - Y2(Cursor2)	Max Y	Min Y	Avg Y
	CURSOR 1,2	V(U1:OUT)	14.815	14.815	0.000	0.000	0.000	14.815	14.815	14.815
		V(R1:2)	-7.7462	-7.7462	0.000	-22.561	-22.561	-7.7462	-7.7462	-7.7462
		I(R1)	-2.2809m	-2.2809m	0.000	-14.817	-14.817	-2.2809m	-2.2809m	-2.2809m
		I(R2)	-2.2809m	-2.2809m	0.000	-14.817	-14.817	-2.2809m	-2.2809m	-2.2809m

Experiment 2

Experiment 2		Calculated	Measured	Simulated			
Vs=-1V	Vo	Vo=8.9101V	Vo=-0.008mV	Vo=-14.815V		Value	Actual Value
	Vx	Vx=-1V	Vx=-0.005mV	Vx=-1.3457V	Resistor 1	1K	0.99810K
	I1	I1=0.50602mA	I1=-1.0009mA	I1=-1.3619mA	Resistor 2	10K	9.89128K
	I2	I2=0.50602mA	I2=-1.0143mA	I2=1.3618mA			
Vs=0.5V	Vo	Vo=4.505V	Vo=0.002mV	Vo=-14.815V			
	Vx	Vx=0.5V	Vx=0.014mV	Vx=-1.3457V			
	I1	I1=0.50602mA	I1=-0.5102mA	I1=-1.3619mA			
	I2	I2=0.50602mA	I2=-0.5119mA	I2=1.3618mA			

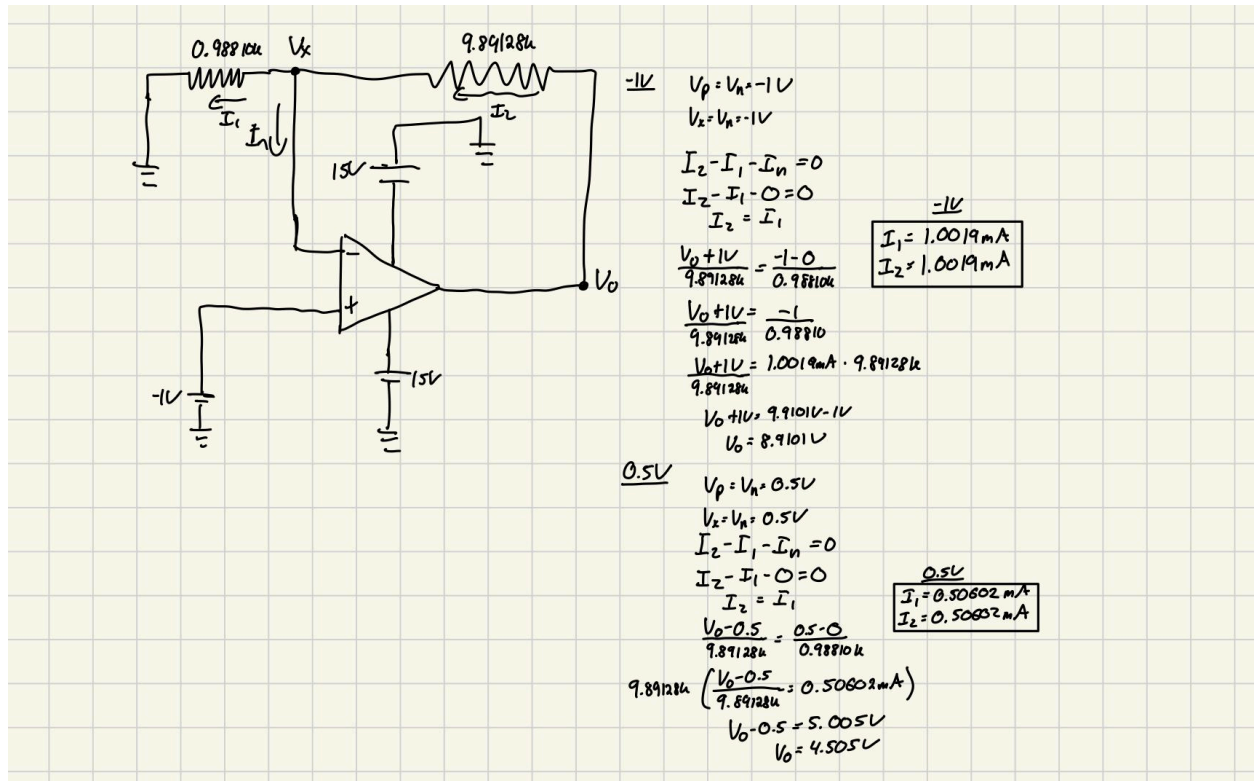

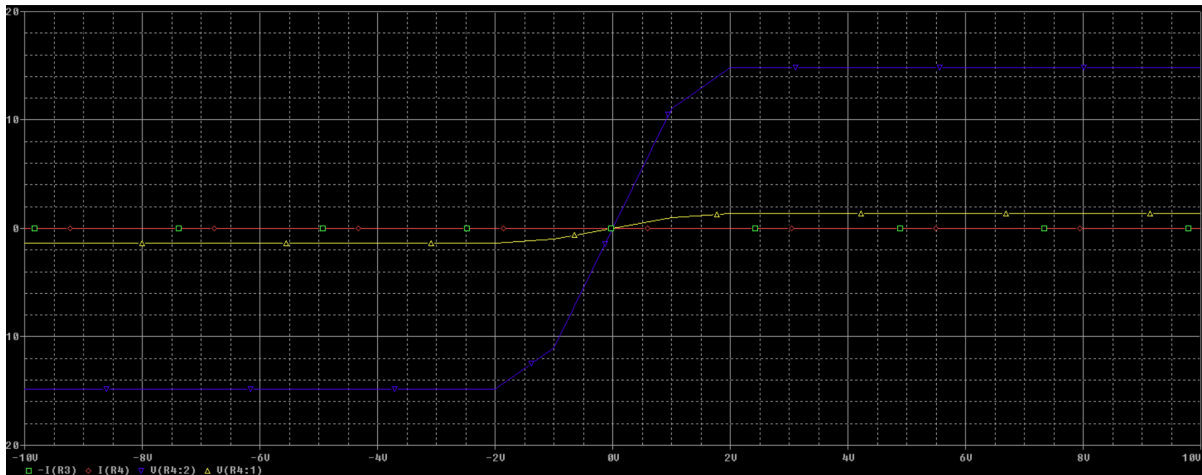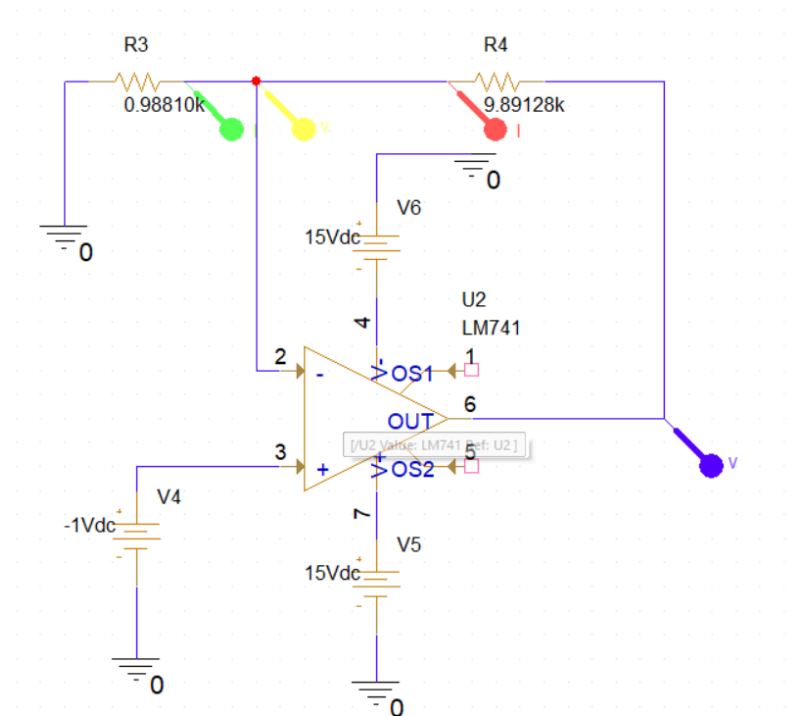

		X Values	-10.000	-10.000	0.000					
	CURSOR 1,2	$-I(R3)$	-1.3619m	-1.3619m	0.000		$Y1 - Y1(\text{Cursor1})$	$Y2 - Y2(\text{Cursor2})$	Max Y	Min Y
		$I(R4)$	1.3618m	1.3618m	0.000		0.000	0.000	-1.3619m	-1.3619m
		$V(R4:2)$	-14.815	-14.815	0.000		2.7237m	2.7237m	1.3618m	1.3618m
		$V(R4:1)$	-1.3457	-1.3457	0.000		-14.814	-14.814	-14.815	-14.815
							-1.3444	-1.3444	-1.3457	-1.3457